

**21EES101T**




**ELECTRICAL AND ELECTRONICS**  
**ENGINEERING**

# **Unit-1**






## **ELECTRIC CIRCUITS**

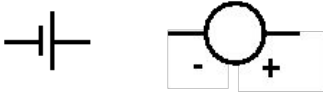Electric circuits are broadly classified as Direct Current (D.C.) circuits and Alternating Current (A.C.) circuits. The following are the various elements that form electric circuits.

### D.C. Circuits

<u>Elements</u>	<u>Representation</u>
Voltage source	
Current source	
Resistor	
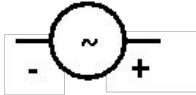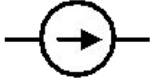
### A.C. Circuits
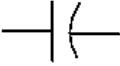
<u>Elements</u>	<u>Representation</u>
Voltage source	
Current source	
Resistor	
Inductor	
Capacitor	

**An active element is capable of generating energy** while a passive element is not.


Typical active elements include generators, batteries and operational amplifiers. Examples of passive elements are resistors, capacitors and inductors. Usually the voltage across a passive element is represented as  $v(t)$  while that across a active element is represented either as  $v(t)$  or  $e(t)$ .

We also will classified sources as **Independent** and **Dependent** sources


**Independent source** establishes a voltage or a current in a circuit without relying on a voltage or current elsewhere in the circuit

**Dependent sources** establishes a voltage or a current in a circuit whose value depends on the value of a voltage or a current elsewhere in the circuit

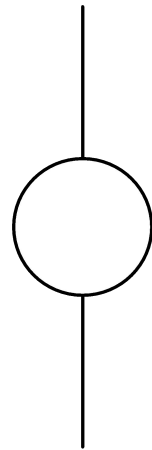We will use circle to represent **Independent source** and diamond shape to represent **Dependent sources**





**Independent source**

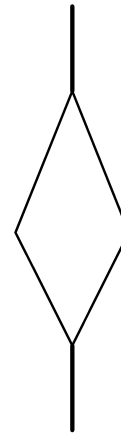


**Dependent sources**
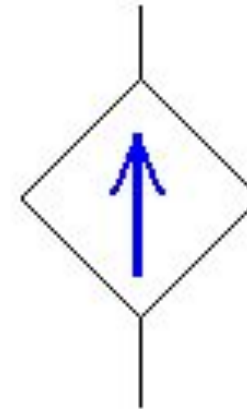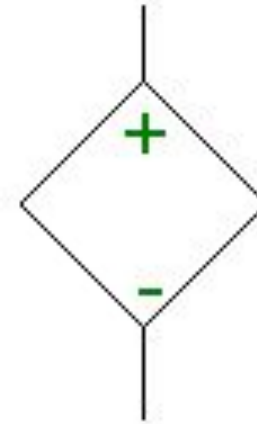
# Dependent Power Sources


- Voltage controlled voltage source
  - (VCVS)
- Current controlled voltage source
  - (CCVS)
- Voltage controlled current source
  - (VCCS)
- Current controlled current source
  - (CCCS)



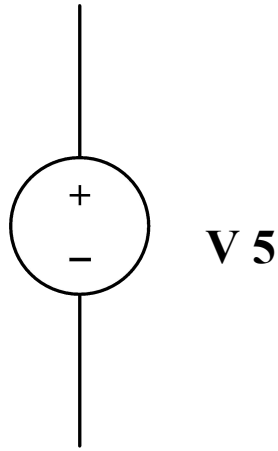
Independent and dependent voltage and current sources can be represented as



Independent voltage source

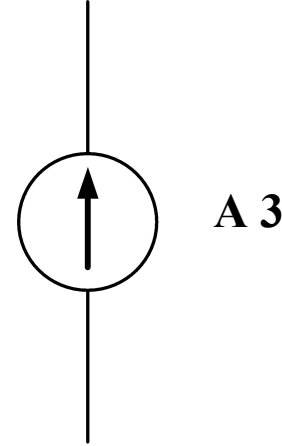


Independent current source

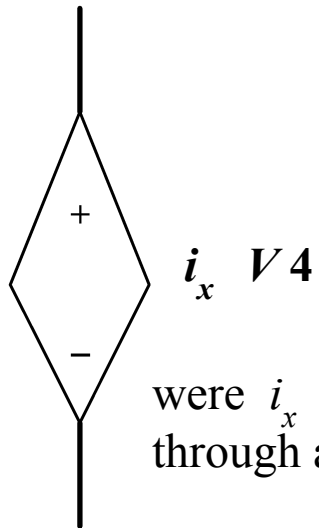

were  $i_x$  is some current  
through an element

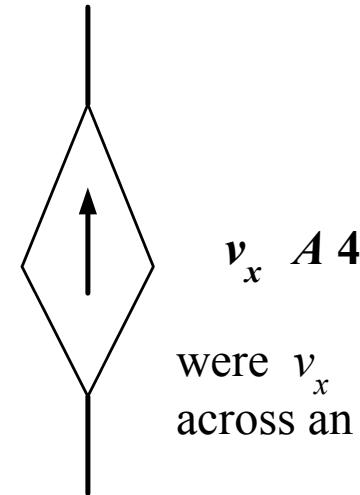
**Dependent voltage source**  
**Voltage depend on current**




were  $v_x$  is some voltage  
across an element

**Dependent current source**  
**Current depend on voltage**

The dependent sources can be also as

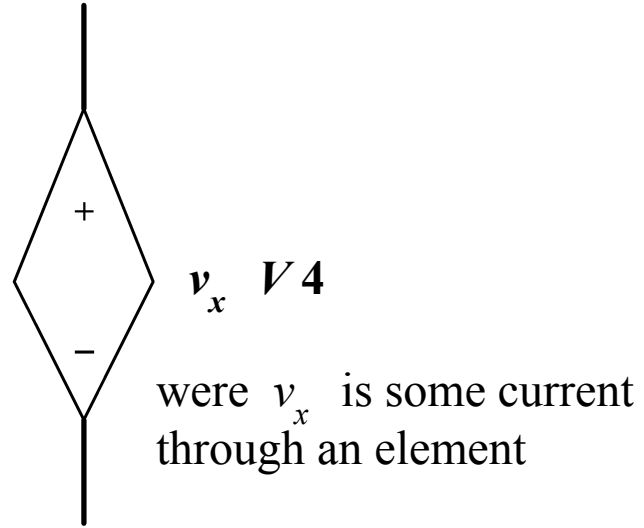

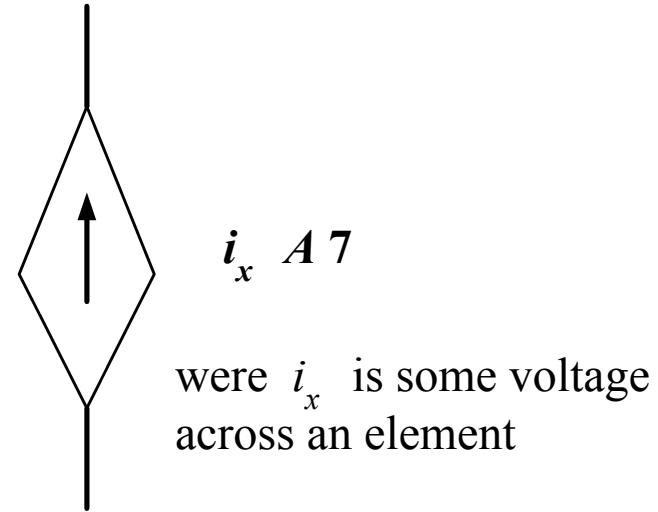**Dependent voltage source**  
**Voltage depend on voltage**




**Dependent current source**  
**Current depend on current**


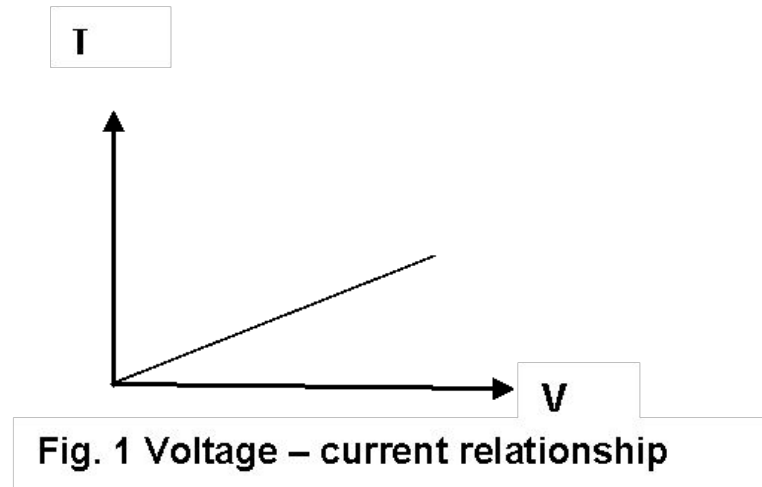
## DC CIRCUITS

The voltage across an element is denoted as  $E$  or  $V$ . The current through the element is  $I$ .

**Conductor is used to carry current.** When a voltage is applied across a conductor, current flows through the conductor. If the applied voltage is increased, the current also increases. The voltage current relationship is shown in Fig. 1.



It is seen that  $I \propto V$ . Thus we can write

$$I = G V \quad (1)$$

where  $G$  is called the conductance of the conductor.

$$I = G V \quad (1)$$

Very often we are more interested on RESISTANCE, R of the conductor, than the conductance of the conductor. **Resistance is the opposing property of the conductor and it is the reciprocal of the conductance.** Thus

$$R = \frac{1}{G} \text{ or } G = \frac{1}{R} \quad (2)$$

$$\text{Therefore } I = \frac{V}{R} \quad (3)$$

The above relationship is known as OHM's law. Thus Ohm law can be stated as the current flows through a conductor is the ratio of the voltage across the conductor and its resistance. Ohm's law can also be written as

$$V = R I \quad (4)$$

$$R = \frac{V}{I} \quad (5)$$

The resistance of a conductor is directly proportional to its length, inversely proportional to its area of cross section. It also depends on the material of the conductor. Thus

$$R = \rho \frac{l}{A} \quad (6)$$

where  $\rho$  is called the specific resistance of the material by which the conductor is made of. The unit of the resistance is Ohm and is represented as  $\Omega$ . Resistance of a conductor depends on the temperature also. The power consumed by the resistor is given by

$$P = V I \quad (7)$$

When the voltage is in volt and the current is in ampere, power will be in watt. Alternate expression for power consumed by the resistors are given below.

$$P = R I \times I = I^2 R \quad (8)$$

$$P = V \times \frac{V}{R} = \frac{V^2}{R} \quad (9)$$

## KIRCHHOFF'S LAWS

There are two Kirchhoff's laws. The first one is called **Kirchhoff's current law, KCL** and the second one is **Kirchhoff's voltage law, KVL**.

Kirchhoff's current law deals with element currents meeting at a junction, which is a meeting point of two or more elements.

Kirchhoff's voltage law deals with element voltages in a closed loop also called as closed circuit.

## Kirchhoff's current law

Kirchhoff's current law states that **the algebraic sum of element currents meeting at a junction is zero.**

Consider a junction P wherein four elements, carrying currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$ , are meeting as shown in Fig. 2.

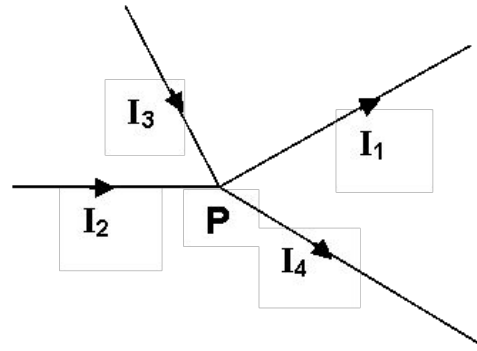


Fig. 2 Currents meeting at a junction

Note that currents  $I_1$  and  $I_4$  are flowing out from the junction while the currents  $I_2$  and  $I_3$  are flowing into the junction. According to KCL,

$$I_1 - I_2 - I_3 + I_4 = 0 \quad (10)$$

The above equation can be rearranged as

$$I_1 + I_4 = I_2 + I_3 \quad (11)$$

From equation (11), KCL can also be stated as **at a junction, the sum of element currents that flows out is equal to the sum of element currents that flows in.**

## Kirchhoff's voltage law

Kirchhoff's voltage law states that the **algebraic sum of element voltages around a closed loop is zero.**

Consider a closed loop in a circuit wherein four elements with voltages  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_4$ , are present as shown in Fig. 3.

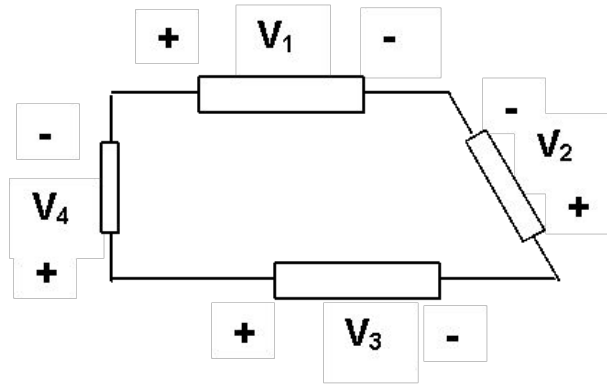


Fig. 3 Voltages in a closed loop

Assigning positive sign for voltage drop and negative sign for voltage rise, when the loop is traced in clockwise direction, according to KVL

$$V_1 - V_2 - V_3 + V_4 = 0 \quad (12)$$

The above equation can be rearranged as

$$V_1 + V_4 = V_2 + V_3 \quad (13)$$

From equation (13), KVL can also be stated as, **in a closed loop, the sum of voltage drops is equal to the sum of voltage rises in that loop.**

## Resistors connected in series

Two resistors are said to be connected in series when there is only one common point between them and no other element is connected in that common point. Resistors connected in series carry same current. Consider three resistors  $R_1$ ,  $R_2$  and  $R_3$  connected in series as shown in Fig. 4. With the supply voltage of  $E$ , voltages across the three resistors are  $V_1$ ,  $V_2$  and  $V_3$ .

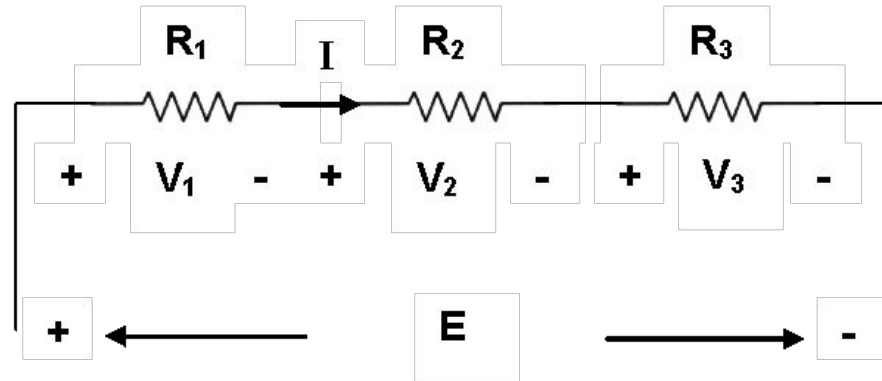


Fig. 4 Resistors connected in series

As per Ohm's law

$$V_1 = R_1 I$$

$$V_2 = R_2 I$$

$$V_3 = R_3 I$$

(14)

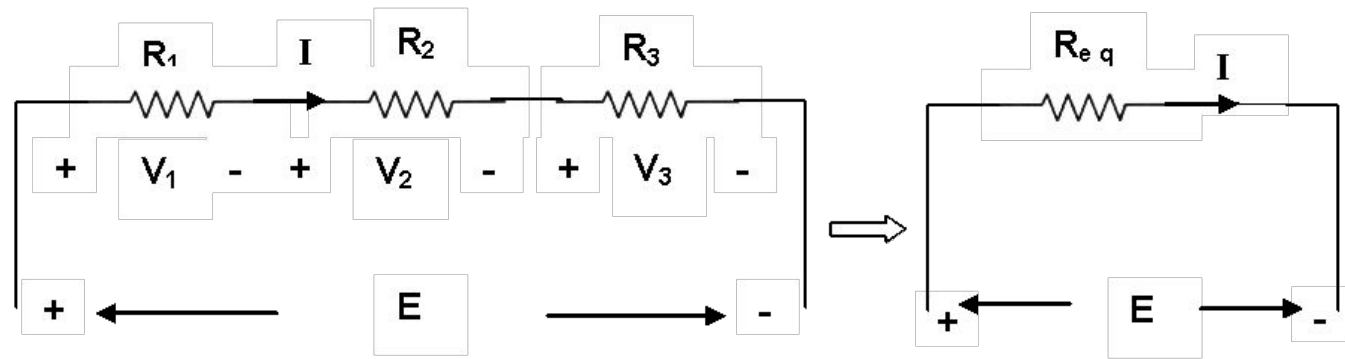


Fig. 4 Resistors connected in series

Applying KVL,

$$E = V_1 + V_2 + V_3 \quad (15)$$

$$= (R_1 + R_2 + R_3) I = R_{eq} I \quad (16)$$

Thus for the circuit shown in Fig. 4,

$$E = R_{eq} I \quad (17)$$

where  $E$  is the circuit voltage,  $I$  is the circuit current and  $R_{eq}$  is the equivalent resistance. Here

$$R_{eq} = R_1 + R_2 + R_3 \quad (18)$$


This is true when two or more resistors are connected in series. When  $n$  numbers of resistors are connected in series, the equivalent resistor is given by

$$R_{eq} = R_1 + R_2 + \dots + R_n \quad (19)$$


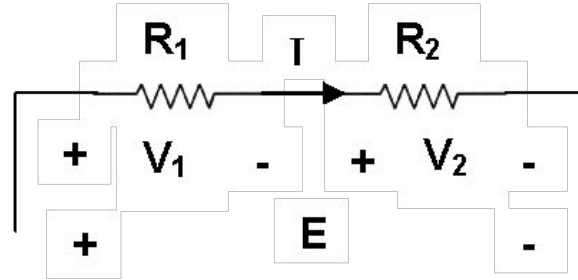
### Voltage division rule

Consider two resistors connected in series. Then



$$V_1 = R_1 I$$

$$V_2 = R_2 I$$

$$E = (R_1 + R_2) I \text{ and hence } I = E / (R_1 + R_2)$$

Total voltage of  $E$  is dropped in two resistors. Voltage across the resistors are given by

$$V_1 = \frac{R_1}{R_1 + R_2} E \quad \text{and} \quad (20)$$

$$V_2 = \frac{R_2}{R_1 + R_2} E \quad (21)$$

## Resistors connected in parallel

**Two resistors are said to be connected in parallel when both are connected across same pair of nodes. Voltages across resistors connected in parallel will be equal.**

**Consider two resistors  $R_1$  and  $R_2$  connected in parallel as shown in Fig. 5.**


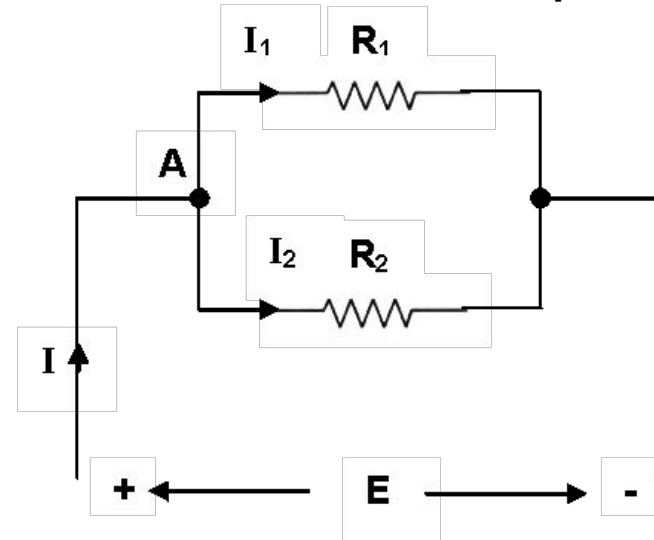


Fig. 5 Resistors connected in parallel

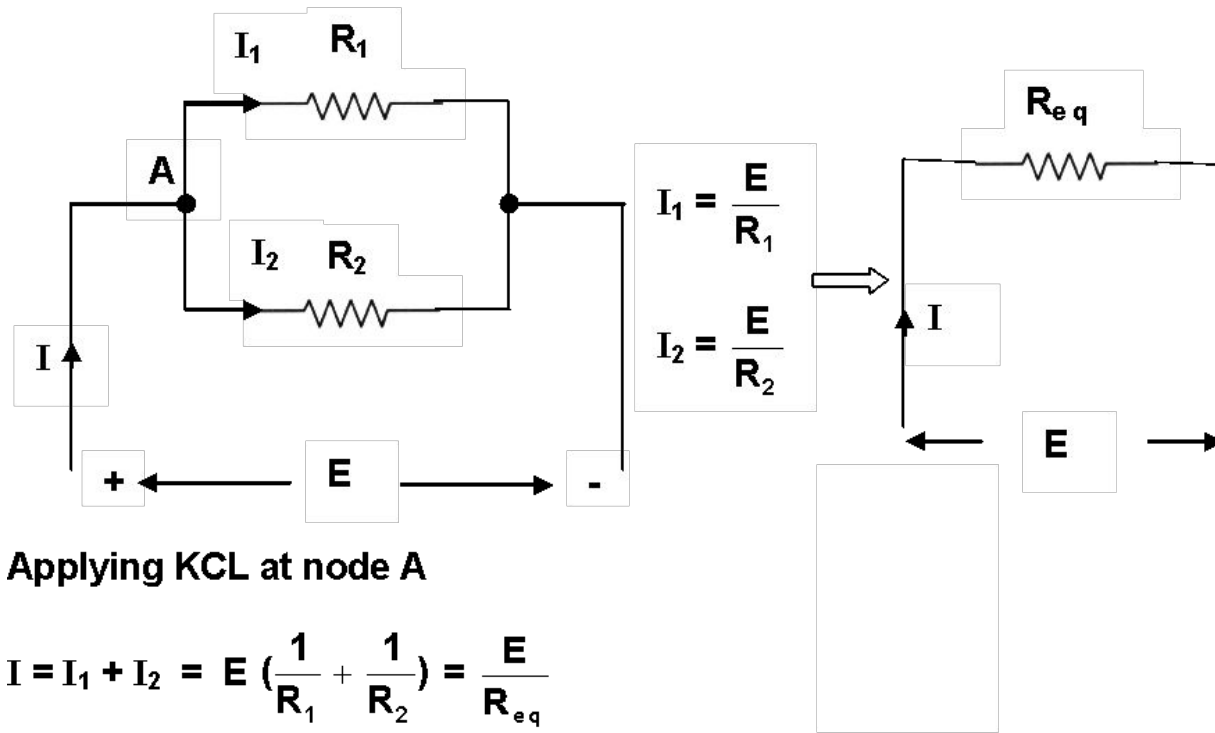**As per Ohm's law,**

$$\left. \begin{aligned} I_1 &= \frac{E}{R_1} \\ I_2 &= \frac{E}{R_2} \end{aligned} \right\}$$



Applying KCL at node A

$$I = I_1 + I_2 = E \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{E}{R_{eq}} \quad (23)$$

Thus for the circuit shown in Fig. 5

$$I = \frac{E}{R_{eq}} \quad (24)$$

where  $E$  is the circuit voltage,  $I$  is the circuit current and  $R_{eq}$  is the equivalent resistance. Here

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (25)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (25)$$


From the above  $\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$

Thus  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad (26)$

When n numbers of resistors are connected in parallel, generalizing eq. (25),  $R_{eq}$  can be obtained from

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \quad (27)$$

### Current division rule

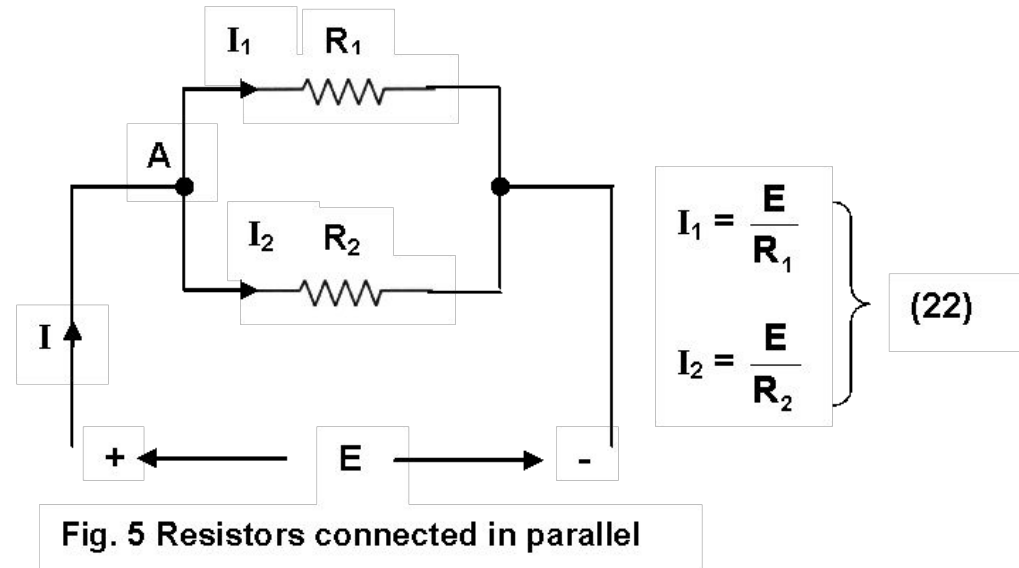

Referring to Fig. 5, it is noticed the total current gets divided as  $I_1$  and  $I_2$ . The branch currents are obtained as follows.

From eq. (23)

$$E = \frac{R_1 R_2}{R_1 + R_2} I \quad (29)$$


Substituting the above in eq. (22)

$$I_1 = \frac{R_2}{R_1 + R_2} I$$
$$I_2 = \frac{R_1}{R_1 + R_2} I \quad (30)$$

### Example 1

Three resistors  $10\Omega$ ,  $20\Omega$  and  $30\Omega$  are connected in series across  $100\text{ V}$  supply.  
Find the voltage across each resistor.

### Solution

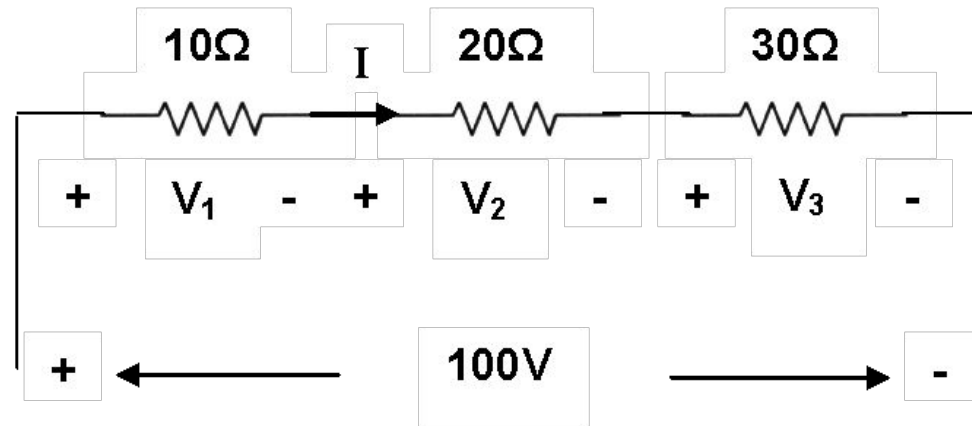

$$\text{Current } I = 100 / (10 + 20 + 30) = 1.6667 \text{ A}$$

$$\text{Voltage across } 10\Omega = 10 \times 1.6667 = 16.67 \text{ V}$$


$$\text{Voltage across } 20\Omega = 20 \times 1.6667 = 33.33 \text{ V}$$

$$\text{Voltage across } 30\Omega = 30 \times 1.6667 = 50 \text{ V}$$

### Example 2

Two resistors of  $4\Omega$  and  $6\Omega$  are connected in parallel. If the supply current is  $30\text{ A}$ , find the current in each resistor.

### Solution

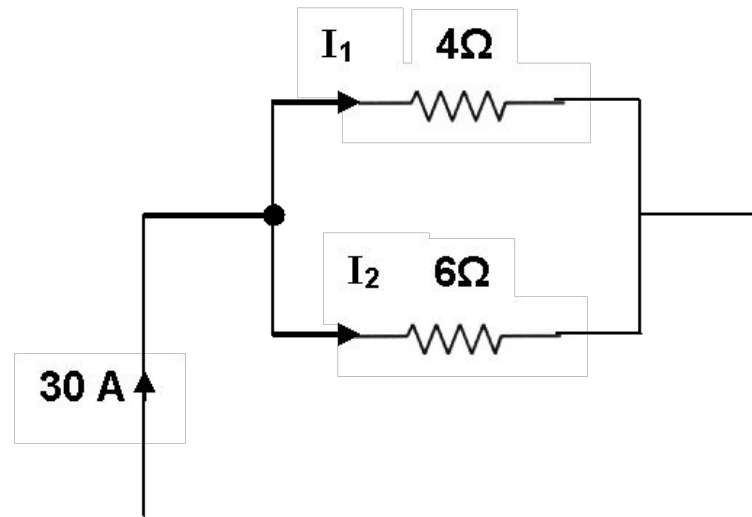

Using the current division rule

$$\text{Current through } 4\Omega = \frac{6}{4 + 6} \times 30 = 18\text{ A}$$

$$\text{Current through } 6\Omega = \frac{4}{4 + 6} \times 30 = 12\text{ A}$$

### Example 3

Four resistors of 2 ohms, 3 ohms, 4 ohms and 5 ohms respectively are connected in parallel. What voltage must be applied to the group in order that the total power of 100 W is absorbed?

### Solution

Let  $R_T$  be the total equivalent resistor. Then

$$\frac{1}{R_T} = \frac{1}{2} + \frac{1}{3} + \frac{1}{4} + \frac{1}{5} = \frac{60+40+30+24}{120} = \frac{154}{120}$$

$$\text{Resistance } R_T = \frac{120}{154} = 0.7792 \Omega$$

Let  $E$  be the supply voltage. Then total current taken =  $E / 0.7792 \text{ A}$

$$\text{Thus } \left(\frac{E}{0.7792}\right)^2 \times 0.7792 = 100 \text{ and hence } E^2 = 100 \times 0.7792 = 77.92$$


$$\text{Required voltage} = \sqrt{77.92} = 8.8272 \text{ V}$$



### Example 4

When a resistor is placed across a 230 V supply, the current is 12 A. What is the value of the resistor that must be placed in parallel, to increase the load to 16 A?

### Solution

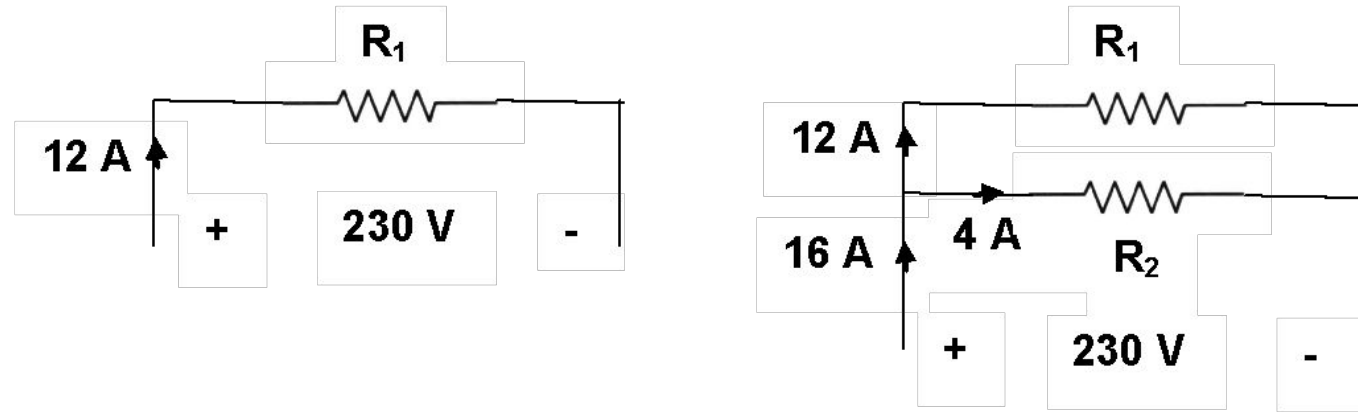



To make the load current 16 A, current through the second resistor =  $16 - 12 = 4$  A

Value of second resistor  $R_2 = 230/4 = 57.5 \Omega$

### Example 5

A  $50\ \Omega$  resistor is in parallel with a  $100\ \Omega$  resistor. The current in  $50\ \Omega$  resistor is  $7.2\text{ A}$ . What is the value of third resistor to be added in parallel to make the line current as  $12.1\text{A}$ ?

### Solution

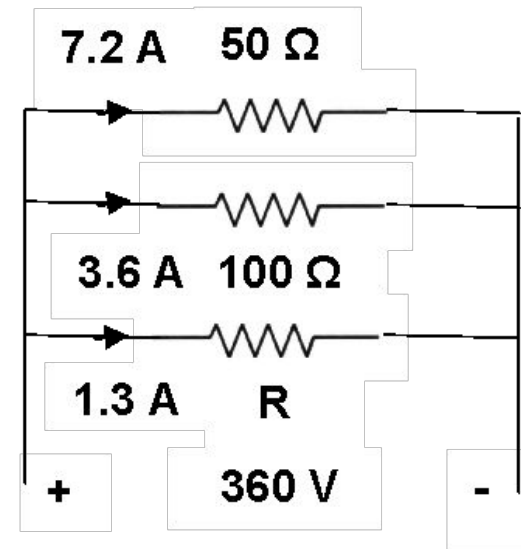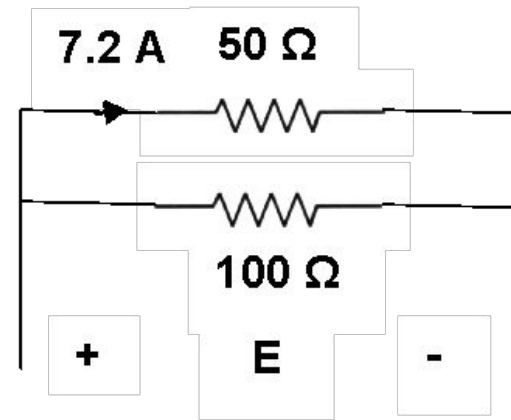

Supply voltage  $E = 50 \times 7.2 = 360\text{ V}$

Current through  $100\ \Omega = 360/100 = 3.6\text{ A}$

When the line current is  $12.1\text{ A}$ , current through third resistor  $= 12.1 - (7.2 + 3.6)$


$$= 1.3\text{ A}$$

Value of third resistor  $= 360/1.3 = 276.9230\ \Omega$

### Example 6

A resistor of 3.6 ohms is connected in series with another of 4.56 ohms. What resistance must be placed across 3.6 ohms, so that the total resistance of the circuit shall be 6 ohms?

### Solution

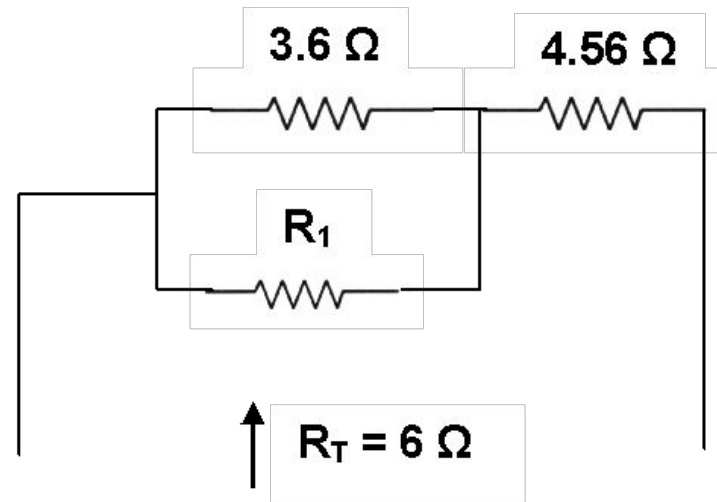

$$3.6 \parallel R_1 = 6 - 4.56 = 1.44 \Omega$$


$$\text{Thus } \frac{3.6 \times R_1}{3.6 + R_1} = 1.44; \quad \text{Therefore } \frac{3.6 + R_1}{R_1} = \frac{3.6}{1.44} = 2.5; \quad \frac{3.6}{R_1} = 1.5$$

$$\text{Required resistance } R_1 = 3.6/1.5 = 2.4 \Omega$$

### Example 7

A resistance  $R$  is connected in series with a parallel circuit comprising two resistors  $12\ \Omega$  and  $8\ \Omega$  respectively. Total power dissipated in the circuit is  $70\text{ W}$  when the applied voltage is  $22\text{ V}$ . Calculate the value of the resistor  $R$ .

### Solution

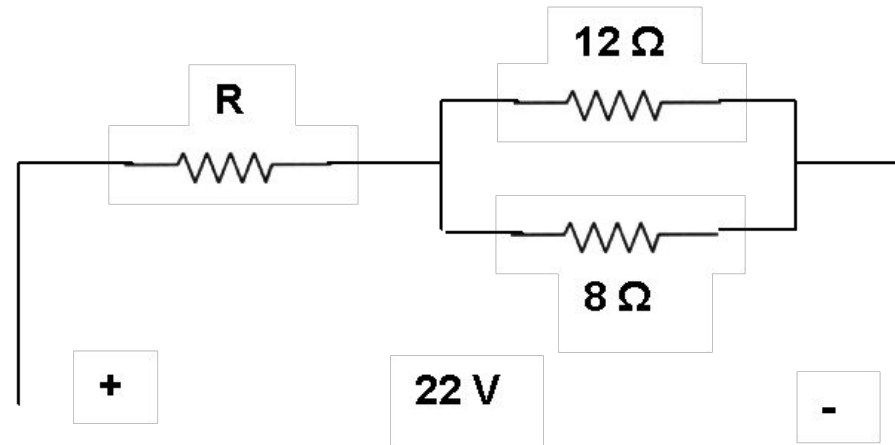

$$\text{Total current taken} = 70 / 22 = 3.1818\text{ A}$$

$$\text{Equivalent of } 12\ \Omega \parallel 8\ \Omega = 96/20 = 4.8\ \Omega$$


$$\text{Voltage across parallel combination} = 4.8 \times 3.1818 = 15.2726\text{ V}$$

$$\text{Voltage across resistor } R = 22 - 15.2726 = 6.7274\text{ V}$$

$$\text{Value of resistor } R = 6.7274/3.1818 = 2.1143\ \Omega$$
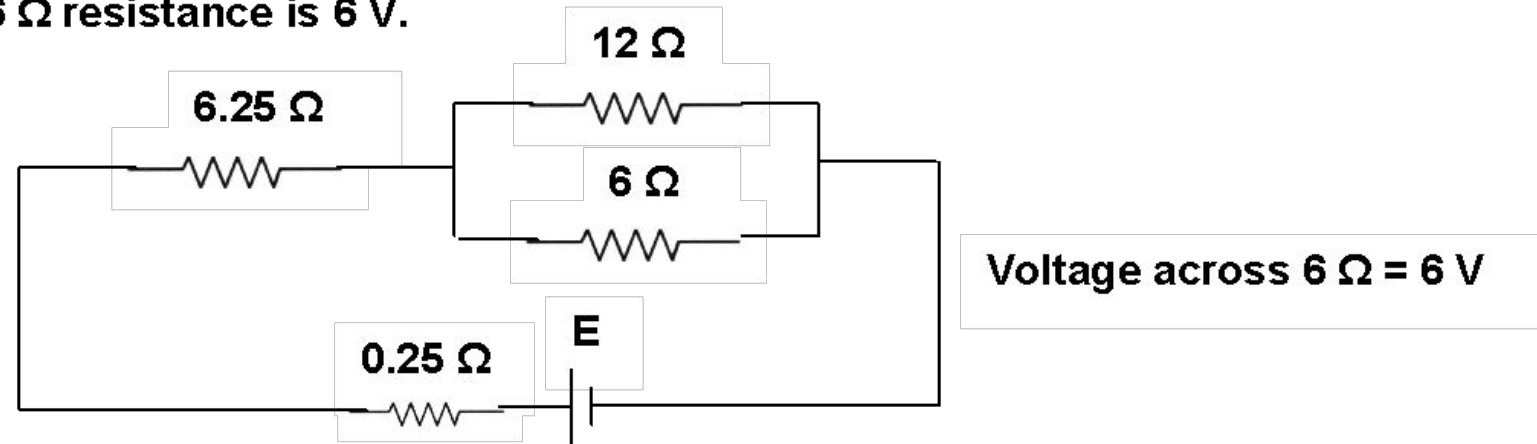
### Example 8

The resistors  $12\ \Omega$  and  $6\ \Omega$  are connected in parallel and this combination is connected in series with a  $6.25\ \Omega$  resistance and a battery which has an internal resistance of  $0.25\ \Omega$ . Determine the emf of the battery if the potential difference across  $6\ \Omega$  resistance is  $6\text{ V}$ .



### Solution

Current in  $6\ \Omega = 6/6 = 1\text{ A}$

Current in  $12\ \Omega = 6/12 = 0.5\text{ A}$

Therefore current in  $0.25\ \Omega = 1.0 + 0.5 = 1.5\text{ A}$


Using KVL  $E = (0.25 \times 1.5) + (6.25 \times 1.5) + 6 = 15.75\text{ V}$

Therefore battery emf  $E = 15.75\text{ V}$

### Example 9

A circuit consist of three resistors  $3\ \Omega$ ,  $4\ \Omega$  and  $6\ \Omega$  in parallel and a fourth resistor of  $4\ \Omega$  in series. A battery of  $12\text{ V}$  and an internal resistance of  $6\ \Omega$  is connected across the circuit. Find the total current in the circuit and the terminal voltage across the battery.

### Solution

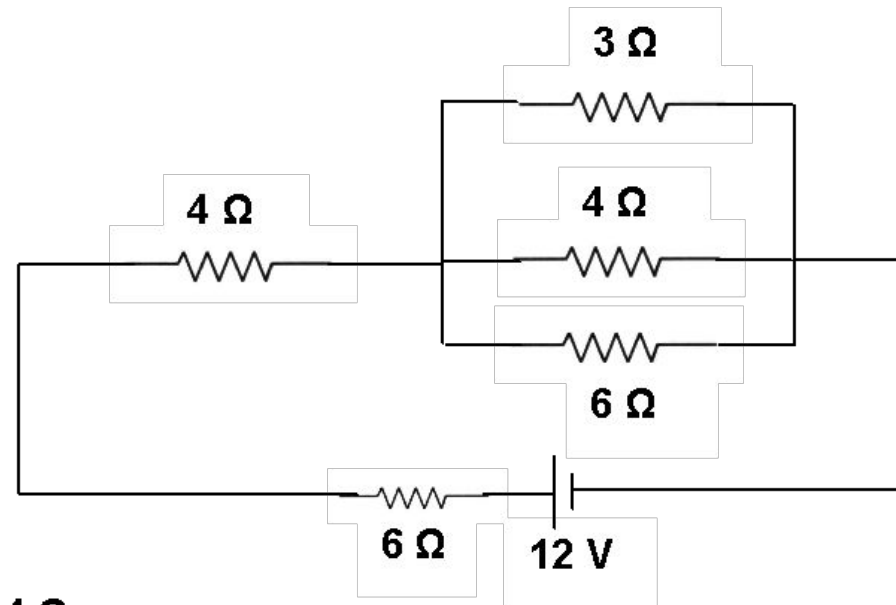

$$4\ \Omega \parallel 6\ \Omega = 24/10 = 2.4\ \Omega$$

$$2.4\ \Omega \parallel 3\ \Omega = 7.2/5.4 = 1.3333\ \Omega$$


$$\text{Total circuit resistance} = 4 + 6 + 1.3333 = 11.3333\ \Omega$$

$$\text{Circuit current} = 12/11.3333 = 1.0588\text{ A}$$

$$\text{Terminal voltage across the battery} = 12 - (6 \times 1.0588) = 5.6472\text{ V}$$


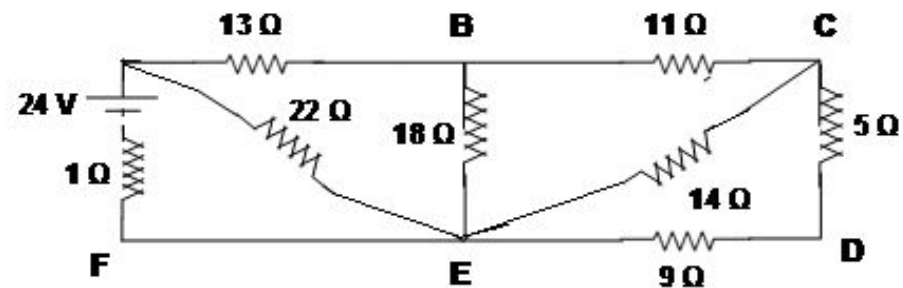
### Example 10


An electrical network is arranged as shown. Find (i) the current in branch AF (ii) the power absorbed in branch BE




### Solution

Various stages of reduction are shown.

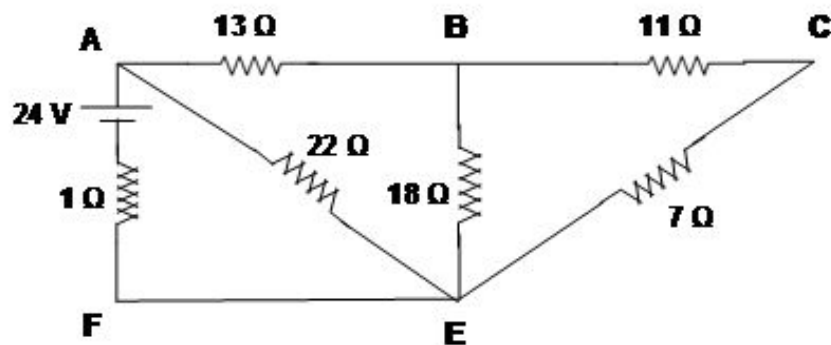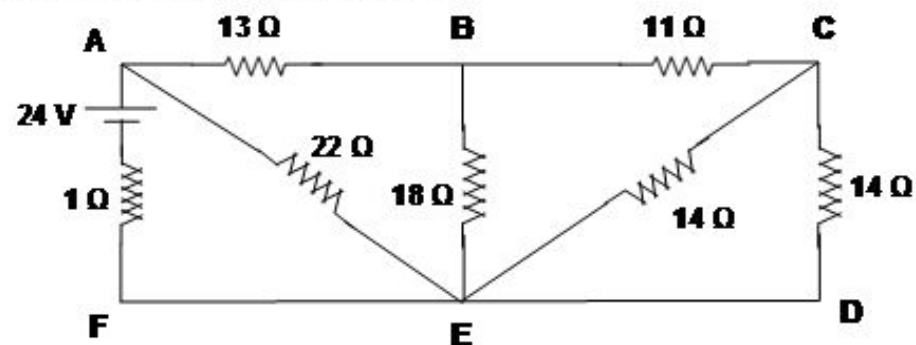

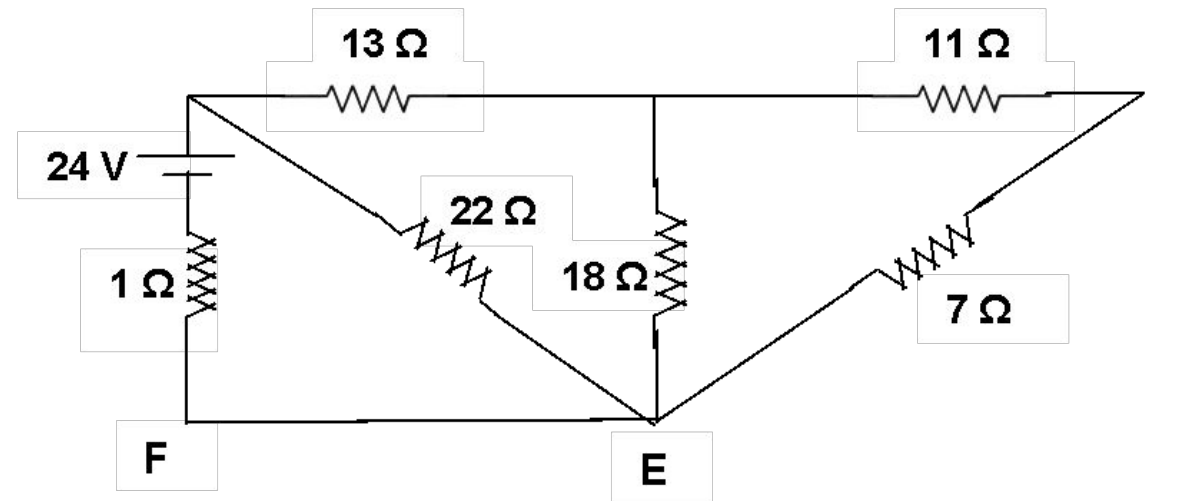


2

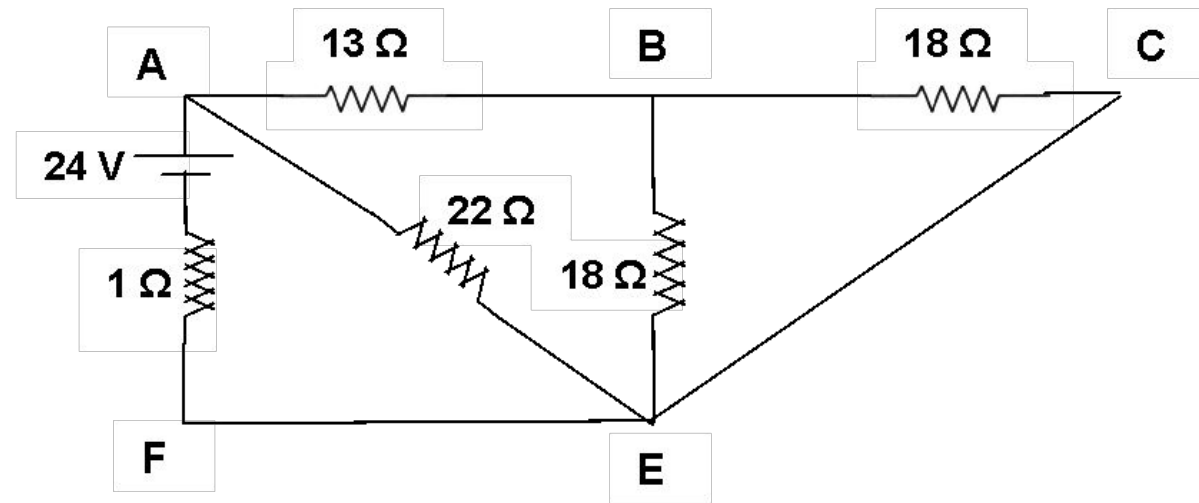


3




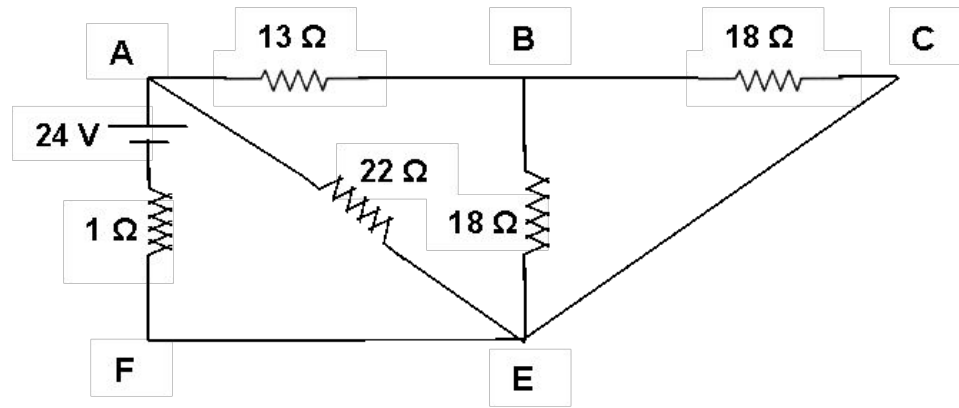


3

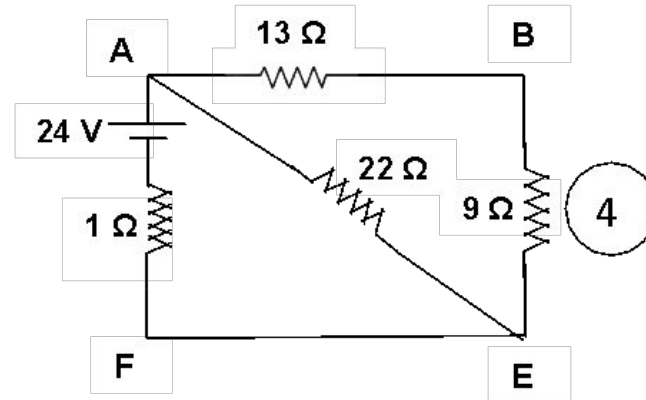

4

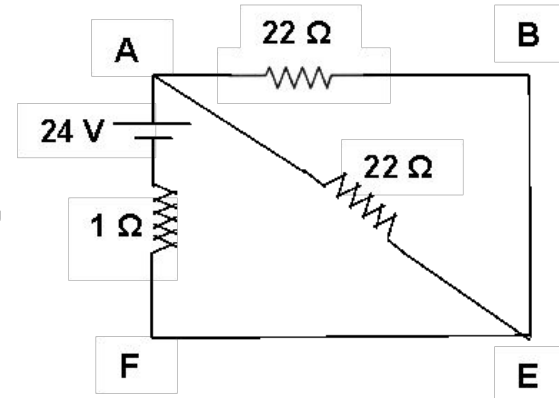

5

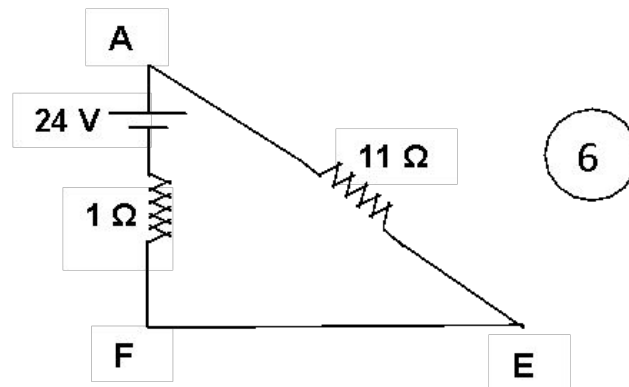

6

Current in branch AF =  $24/12 = 2$  A from F to A

Using current division rule current in  $13\ \Omega$  in Fig. 4 = 1 A

Referring Fig. 3, current in branch BE = 0.5 A

Power absorbed in branch BE =  $0.5^2 \times 18 = 4.5$  W

### 3.2 MESH CURRENT METHOD (ALSO KNOWN AS LOOP ANALYSIS)

Element currents are there in reality while mesh currents are more useful and are imaginary. In any circuit, number of elements and hence the number of element currents, will be larger as compared to the number of independent meshes. All the elements currents can be calculated once we know the mesh currents. Here after independent meshes will be simply referred as meshes and independent mesh currents will be referred as mesh currents leaving the adjective independent.

Consider the circuit shown in Fig. 3.2. This circuit has two meshes and one set of mesh currents are marked.


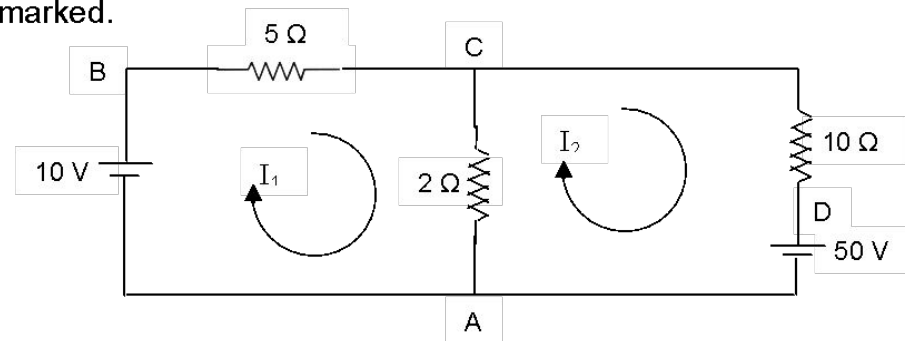


Fig. 3.2 Circuit with two meshes.

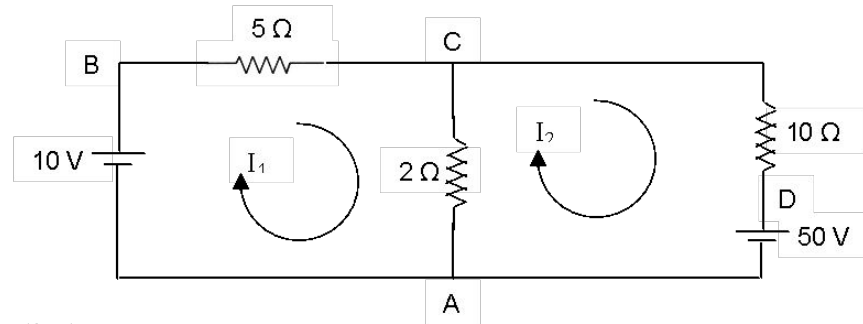

It can be seen that

Current in 10 V battery is  $I_1$  from A to B;

Current in  $5\ \Omega$  resistor is  $I_1$  from B to C;

Current in  $2\ \Omega$  resistor is  $I_1 - I_2$  from C to A or  $I_2 - I_1$  from A to C;

Current in  $10\ \Omega$  is  $I_2$  from C to D; and

Current in 50 V battery is  $I_2$  from D to A or  $-I_2$  from A to D.

Thus all the five element currents can be calculated from the two mesh currents. This is true for any general circuit.

Now let us apply KVL and write the mesh equations for the two meshes. Voltage rises are taken as positive and voltage drops are taken as negative.

$$-10 + 5 I_1 + 2 (I_1 - I_2) = 0 \quad (3.1)$$

$$10 I_2 + 50 + 2 (I_2 - I_1) = 0 \quad (3.2)$$

$$-10 + 5 I_1 + 2 (I_1 - I_2) = 0 \quad (3.1)$$

$$10 I_2 + 50 + 2 (I_2 - I_1) = 0 \quad (3.2)$$

The above equations can be rearranged as

$$7 I_1 - 2 I_2 = 10 \quad (3.3)$$

$$-2 I_1 + 12 I_2 = -50 \quad (3.4)$$

Solving these equations, we get  $I_1 = 0.25 \text{ A}$  and  $I_2 = -4.125 \text{ A}$

The currents in different elements are shown in Fig. 3.3.


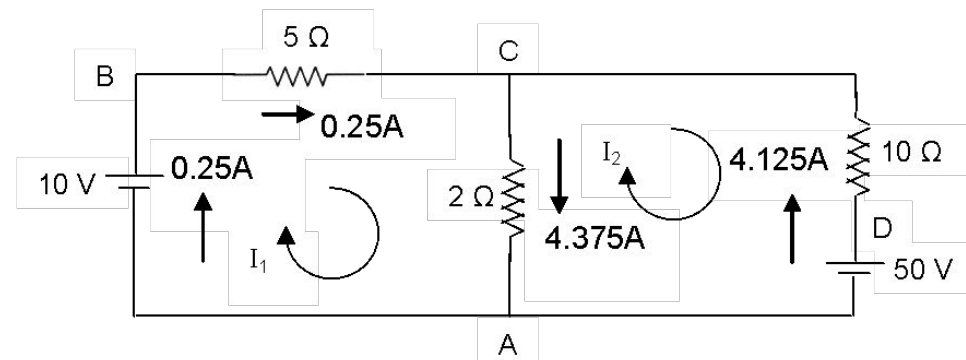


Fig. 3.3 Currents in different elements.

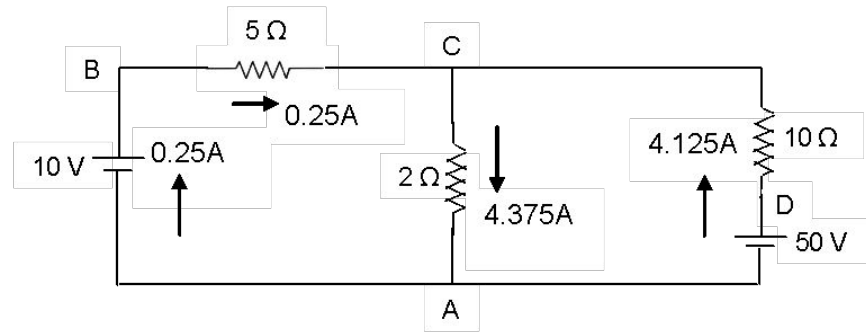

Powers associated with different elements are obtained as:

$$\text{Power consumed by } 5\ \Omega \text{ resistor} = 0.25^2 \times 5 = 0.3125\ \text{W}$$

$$\text{Power consumed by } 2\ \Omega \text{ resistor} = 4.375^2 \times 2 = 38.28125\ \text{W}$$

$$\text{Power consumed by } 10\ \Omega \text{ resistor} = 4.125^2 \times 10 = 170.15625\ \text{W}$$

$$\text{Total power consumed by the resistors} = 208.75\ \text{W}$$

$$\text{Power supplied by } 10\ \text{V battery} = 10 \times 0.25 = 2.5\ \text{W}$$

$$\text{Power supplied by } 50\ \text{V battery} = 50 \times 4.125 = 206.25\ \text{W}$$

$$\text{Total power supplied by the batteries} = 208.75\ \text{W}$$

The following procedure can be followed to solve circuits using mesh current method.

1. Find the number of independent meshes and identify one set of independent meshes.
2. Assume either clockwise or anti-clockwise direction for the mesh currents in the independent meshes. Once the mesh currents are assumed, element currents in the required direction can be obtained in terms of the mesh currents.
3. For each independent mesh, travel through the elements in the assumed mesh current direction and write the equation applying KVL.
4. Solve these equations for the mesh currents.

Other quantities of interest can now be computed.

### Example 3.1

For the circuit shown in Fig. 3.4 (i) compute the mesh currents (ii) determine the total power loss in the resistors and (iii) find the power associated with the voltage sources and the total power supplied by them.

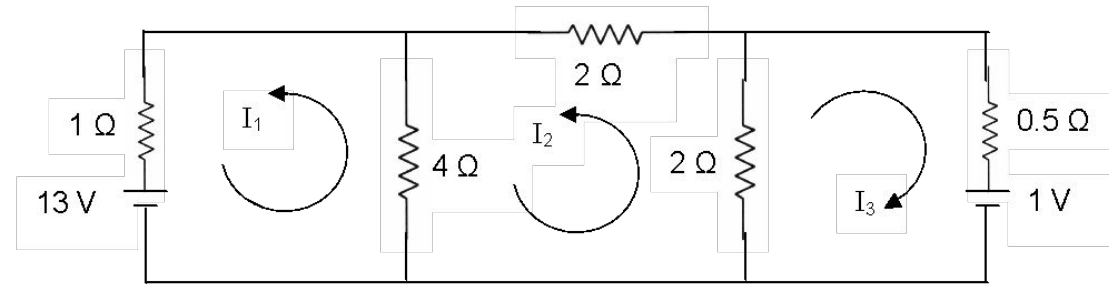


Fig. 3.4 Circuit for Example 3.1.

### Solution:


Three mesh equations can be obtained as:

$$I_1 + 13 + 4(I_1 - I_2) = 0 \text{ i.e. } 5 I_1 - 4 I_2 = -13$$

$$2 I_2 + 4(I_2 - I_1) + 2(I_2 + I_3) = 0 \text{ i.e. } -4 I_1 + 8 I_2 + 2 I_3 = 0$$
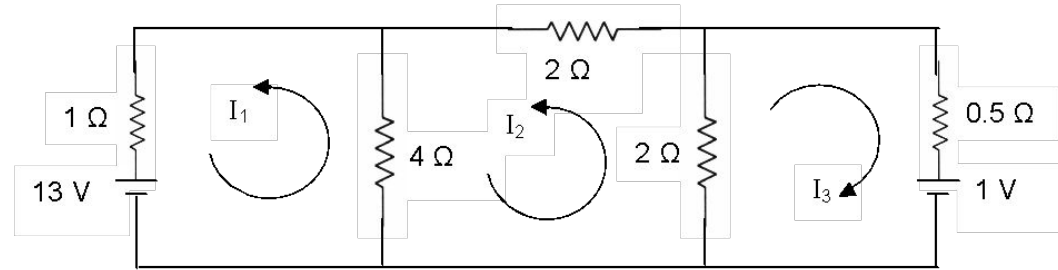
$$0.5 I_3 + 1 + 2(I_3 + I_2) = 0 \text{ i.e. } 2 I_2 + 2.5 I_3 = -1$$





Matrix form of the mesh equations is

$$\begin{bmatrix} 5 & -4 & 0 \\ -4 & 8 & 2 \\ 0 & 2 & 2.5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -13 \\ 0 \\ -1 \end{bmatrix}$$

Mesh currents are:  $I_1 = -5 \text{ A}$ ;  $I_2 = -3 \text{ A}$ ;  $I_3 = 2 \text{ A}$

**When the circuit contains only independent voltage sources, mesh equations in matrix form can be written directly by examining the circuit.**

Total power loss =  $25 + 16 + 18 + 2 + 2 = 63 \text{ W}$

Power supplied by 13 V battery = 65 W ;

It is to be noted that in 1 V battery, positive current leaves the negative terminal.

Therefore, power received by 1 V battery = 2 W

Thus 13 V battery is in discharge mode whereas 1 V battery is in charge mode.